Present State		Input	Next State		Output
Α	В	x	Α	В	У
0	0	1	0	0	1
0	0	0	0	1	0
0	1	0	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	0	1	0
1	1	1	1	0	1
1	1	0	1	1	0

//	0	1
00	01/0	00/1
01	10/1	11/0
11	11/0	10/1
10	00/1	01/0

//	0	1
00	0	0
01	1	1
11	1	1
10	0	0

//	0	1
00	1	0
01	0	1
11	1	0
10	0	1

//	0	1
00	0	1
01	1	0
11	0	1
10	1	0